

#1 Calculation of equivalent circuit parameters from tests for I.M.

The following test results are obtained from a 3-phase, 60 hp, 2200 V, 6 pole, 50 Hz, Star connected squirrel-cage I.M.

i) No-load test:

Line voltage = 2200 V

Supply frequency = 50 Hz

Line current = 4.5 A

Input power = 1600 W

ii) Blocked-rotor test:

Frequency = 12.5 Hz

Line voltage = 270 V

Line current = 25 A

Input power = 9000 W

iii) Resistance between two terminals = 5.6Ω .
Ignore skin effect.

a) Determine the equivalent circuit parameters

b) Determine no-load rotational losses including core-losses.


c) Analyse the performance of the motor.

i) DC resistance:

$$R_1 = \frac{5.6}{2} = 2.8 \Omega$$

$$R_{1,AC} = R_{1,DC} = 2.8 \Omega$$

(ignoring skin effect)

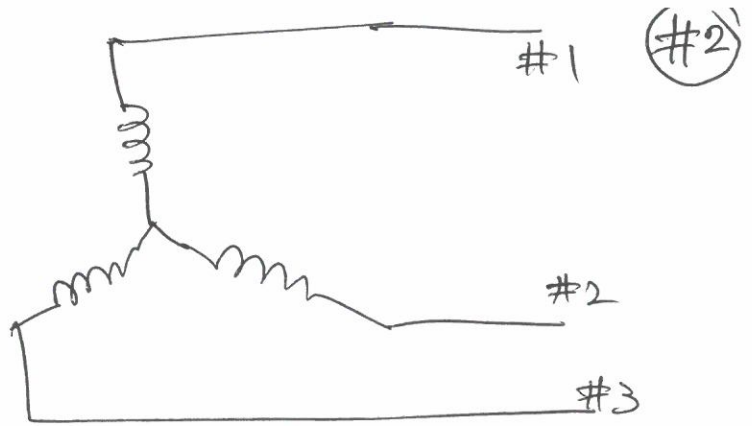

ii) Blocked-rotor test.

$$V_{BL} = \frac{270}{\sqrt{3}} = 155.88 V$$

$$I_{BL} = 25 A$$

$$Z_{BL} = \frac{V_{BL}}{I_{BL}} = 6.24 \Omega$$

$$R_{BL} = \frac{P_{BL}}{3 I_{BL}^2} = \frac{9000}{3 \times 25^2} = 4.8 \Omega$$

$$R_2 = R_{BL} - R_1 = 4.8 - 2.8 = 2.0 \Omega$$

The blocked-rotor reactance at 12.5 Hz

$$X_{BL} = \sqrt{Z_{BL}^2 - R_{BL}^2} = \sqrt{(6.24)^2 - (4.8)^2} = 3.98 \Omega$$

$$X_{BL} \text{ at } 50 \text{ Hz} = \frac{50}{12.5} \times 3.98 = 15.92 \Omega$$



$$\text{Hence, } X_1 = X_2 = \frac{X_{BL}}{2} = \frac{15.92}{2} = 7.96 \Omega$$

iii) No-load test:

$$V_{NL} = \frac{2200}{\sqrt{3}} = 1270.2 V$$

$$I_{NL} = 4.5 A$$

$$P_{NL} = 1600 W$$

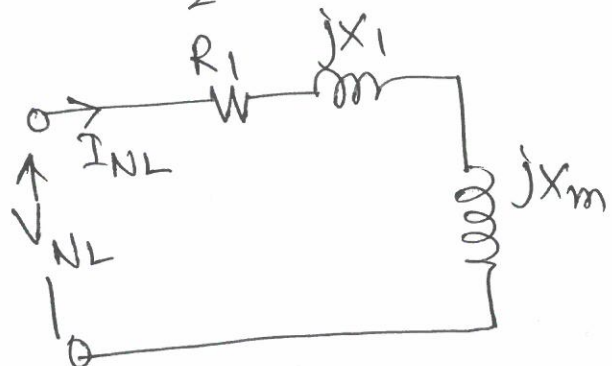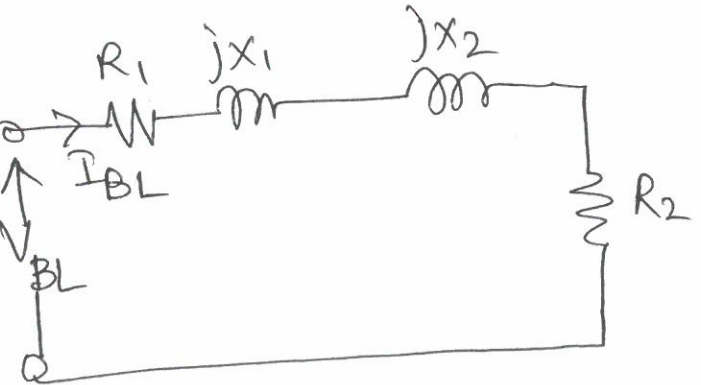

$$Z_{NL} = \frac{V_{NL}}{I_{NL}} = \frac{1270.2}{4.5} = 282.27 \Omega$$

#3

No-load resistance,

$$R_{NL} = \frac{P_{NL}}{3I_{NL}^2} = \frac{1600}{3 \times (4.5)^2} = 26.34 \Omega$$


No-load reactance

$$X_{NL} = \sqrt{Z_{NL}^2 - R_{NL}^2} = \sqrt{(282.27)^2 - (26.34)^2}$$

$$= 281.0 \Omega$$

$$\text{So, } X_m = X_{NL} - X_1 = 281.0 - 7.96 = 273.04 \Omega$$

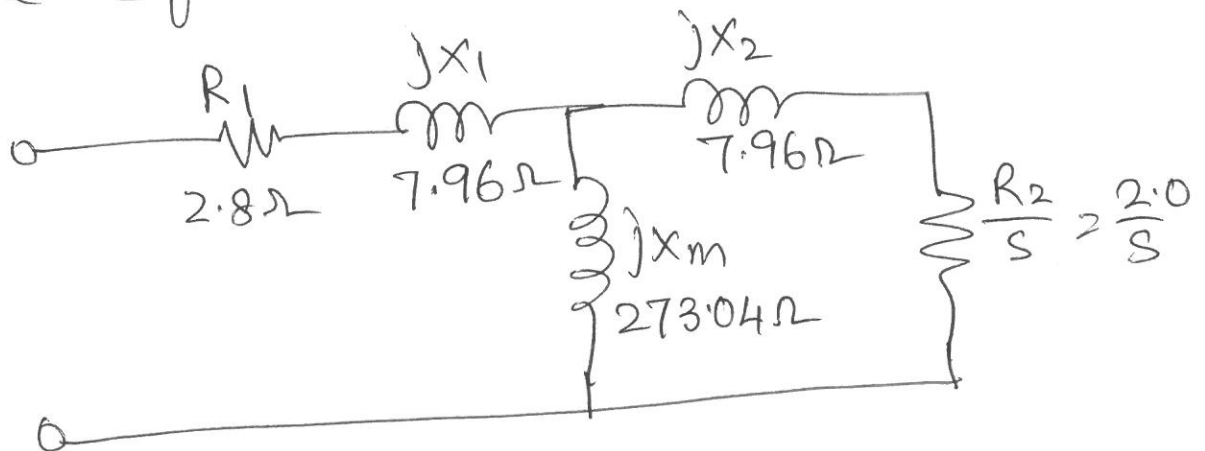— So the equivalent circuit parameters are



$$\text{No load power} = 1600 \text{ W}$$

Rotational losses including core losses

$$= P_{NL} - 3 I_1^2 R_1$$

$$= 1600 - 3 \times (4.5)^2 \times 2.8$$


$$= 1429.9 \text{ W}$$

Assuming the full load slip as 5%, the

analysis can be carried out as given.

$$N_r = (1-s)N_s = (1-0.05) \times 1000 = 950 \text{ rpm}$$

#4

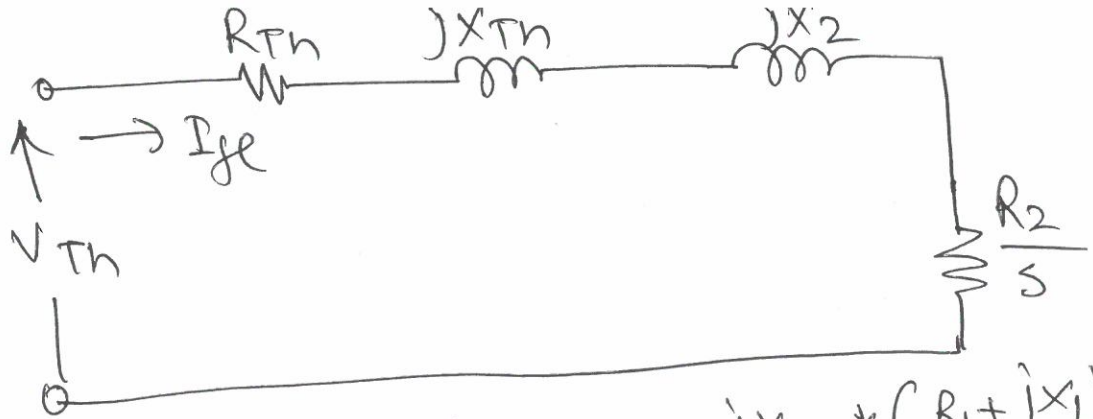

$$R_{Th} + jX_{Th} = (R_1 + jX_1) \parallel jX_m = \frac{jX_m * (R_1 + jX_1)}{R_1 + j(X_1 + X_m)}$$

$$= \frac{j 273.04 * (2.8 + j7.96)}{2.8 + j281}$$

$$= \frac{273.04 \angle 90^\circ * 8.438 \angle 70.62^\circ}{281.01 \angle 89.43^\circ}$$

$$= 8.198 \angle 71.19^\circ$$

$$= 2.643 + j7.76$$

$$V_{Th} = \frac{jX_m}{R_1 + j(X_1 + X_m)} * V_1 = \frac{j 273.04}{2.8 + j281} * 1270.2$$

$$= 1234.17 \text{ V}$$

$$I_{fl} = \frac{V_{Th}}{(R_{Th} + \frac{R_2}{s}) + j(X_{Th} + X_2)}$$

$$= \frac{1234.17}{(2.643 + \frac{2}{0.05}) + j(7.76 + 7.96)}$$

$$= \frac{1234.17}{42.634 + j15.72}$$

$$= \frac{1234.17}{45.44 \angle 20.24^\circ} = 27.16 \angle -20.24^\circ$$

#5

Full load current,

$$I_L = I_{ph} = 27.16 \text{ A (Star-connected)}$$

Full load power factor

$$\cos(20.24^\circ) = 0.938$$

Full load Input power

$$\begin{aligned} P_{in} &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} * 2200 * 27.16 * 0.938 \\ &= 97076.9 \text{ W} \end{aligned}$$

Full load stator cu loss

$$\begin{aligned} P_{cu} &= 3 I_{fl}^2 \cdot R_1 = 3 * (27.16)^2 * 2.8 \\ &= 6196.39 \text{ W} \end{aligned}$$

Full load air-gap power

$$\begin{aligned} P_{ag} &= P_{in} - P_{cu} \quad (\text{ignoring stator core loss}) \\ &= 97076.9 - 6196.39 \\ &= 90880.5 \text{ W} \end{aligned}$$

Full load rotor cu loss

$$P_{rotor} = s P_{ag} = 0.05 * 90880.5 = 4544.0 \text{ W}$$

Full load power developed

$$\begin{aligned} P_{dev} &= P_{ag} - P_{rotor} = 90880.5 - 4544.0 \\ &= 86336.5 \text{ W} \end{aligned}$$

$$\begin{aligned} P_{out} &= P_{dev} - P_{rotational} = 86336.5 - 1429.9 \\ &= 84906.6 \text{ W} \end{aligned}$$

$$\eta = \frac{P_{out}}{P_{in}} * 100 = \frac{84906.6}{97076.9} * 100 = 87.46\%$$

$$T_{fl} = \frac{P_{out}}{\omega} = \frac{84906.6}{2\pi * \frac{950}{60}} = 853.47 \text{ N-m.}$$

#6 By changing the value of slip, s (which means the motor runs at different speeds) it is possible to determine all parameters.

⊙ The performance parameters are determined without doing actual load test.

Due to this reason equivalent circuit parameters are very useful.

