





MACQUARIE
University

ELEC2005

Electrical and Electronic Systems

INTRODUCTION AND PREREQUISITE REVIEW

DAVID PAYNE

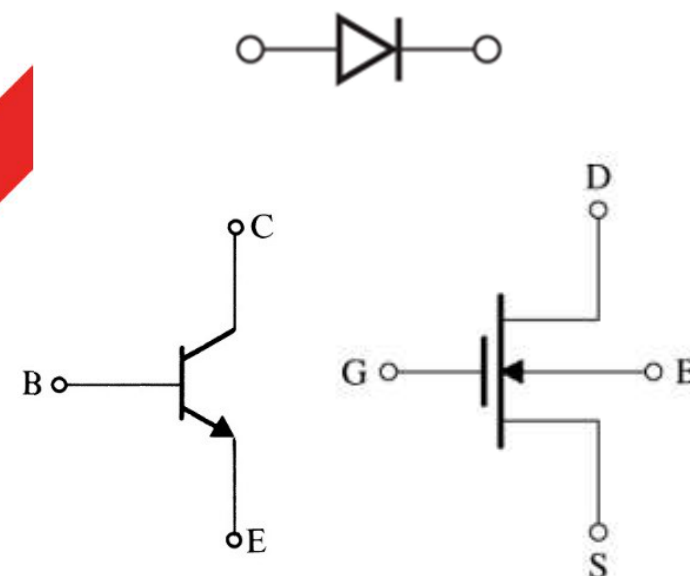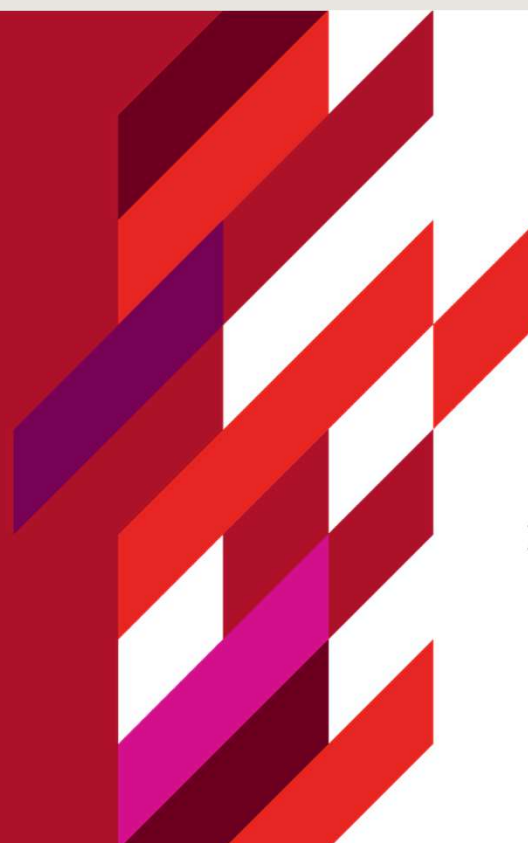



Lecture 1

1. **Unit Overview**
2. Review of fundamental concepts
3. Nonlinearity
4. Amplifiers

Teaching Staff

Unit Conveners:

Dr. David Payne

David.payne@mq.edu.au



Dr. Leonardo Callegaro

leonardo.callegaro@mq.edu.au



Tutor:

Tutors will also be available in the lab sessions and tutorial workshops.

**Please read the
unit guide!**

-
- These lectures topics are covered in the following textbooks:

Microelectronic Circuits

Sedra/Smith, 6th Edition

Power system analysis & design

Glover/Overbye/Sarma, 6th Edition

Power electronics: a first course

Mohan

Two Parts to this Unit

Part 1: Weeks 1-7 Nonlinear Devices

Diodes, BJTs, MOSFETs

How do they **work**?

How do we use them in **circuits**?


Building circuits to specifications (circuit **design**)

Developing a “library” of **building blocks** and...

Building our **experience**!

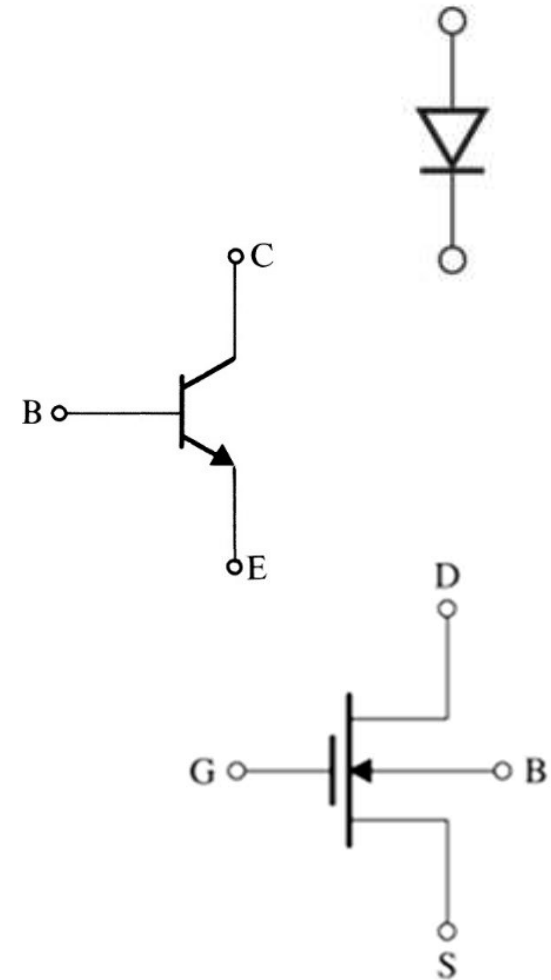Part 2: Weeks 8-13

High power systems and components, energy generation/conversion/storage



Weekly plan, part 1

Week	Lecture date <u>Tuesday</u>	Lecture Topics	Staff	Book chapters	Assignment	Laboratory/workshop session	Lab/ workshop location
1	25/07/23	Unit overview, prereq review, circuit analysis and amplifiers.	DP	Sedra Ch. 1.1-1.5, 2		No laboratory or workshop session	44 Waterloo Rd, Room G65
2	01/08/23	Non-linearity, Diodes, diode models and circuits	DP	Sedra Ch. 3		Lab 1: Introduction to LTspice and Analog Discovery Kits	44 Waterloo Rd, Room G65
3	08/08/23	BJT concepts, models. Intro theory	DP	Sedra Ch. 4	Assign 1 posted	Lab 2: Diode Circuits	44 Waterloo Rd, Room G65
4	15/08/23 Submit Assign 1	BJT large-signal and small-signal analysis	DP	Sedra Ch. 4		Tutorial Workshop 1: Diodes and BJTs	44 Waterloo Rd, Room G65
5	22/08/23	MOSFET concepts, models. Intro theory	DP	Sedra Ch. 5	Assign 1 due	Lab 3: BJT Amplifier	44 Waterloo Rd, Room G65
6	29/08/23 Submit Assign 2	MOSFET Circuits, large-signal and small-signal analysis	DP	Sedra Ch. 5	Assign 2 posted	Lab 4: MOSFET Amplifier	44 Waterloo Rd, Room G65
7	05/09/23	Power Semiconductors, Thyristors, IGBT	DP	Mohan Ch.2.1-2.4		Tutorial Workshop 2: MOSFETS and Power Semiconductors	44 Waterloo Rd, Room G65

Weekly plan, part 2

8	26/09/23	AC circuits review, PFC: Ohm's law, KCL, KVL, series, parallel, time-domain AC power, phasors, impedance, power factor, power triangle, power factor correction (PFC)	LC	Lecture slides, Glover Ch. 2	Assign 2 due	Lab 5: Single-phase ac circuits	44 Waterloo Rd, Room G18
9	03/10/23	Three-phase systems: 3 ϕ power, <u>star</u> and delta connections, balanced and unbalanced 3 ϕ systems	LC	Lecture slides, Glover Ch. 2	Assign 3 <u>posted</u>	Lab 6: Power factor correction	44 Waterloo Rd, Room G18
10	10/10/23	<u>Magnetics and transformer</u> : Review of magnetic circuits, inductance calculation, power transformer principles	LC	Lecture slides, Mohan Ch. 7, Glover Ch. 3	Assign 3 <u>due</u>	Tutorial Workshop 3: Single and three-phase ac circuits, power calculation, power factor correction	44 Waterloo Rd, Room G18
11	17/10/23	<u>Principles of renewable-energy based power systems</u> : renewables, PV energy & power conversion	LC	Lecture slides, (<u>Masters</u> Ch. 8 -)	Assign 4 <u>posted</u>	Lab 7: Single-phase transformer	44 Waterloo Rd, Room G18
12	24/10/23	Principles of battery energy storage and electric vehicles	LC	Lecture slides, (<u>Masters</u> Ch. 9 -; <u>LabVolt</u> Battery Manual)		Lab 8: Three-phase circuits	44 Waterloo Rd, Room G18
13	31/10/23	Review Lecture	LC		Assign 4 due	Tutorial Workshop 4: Magnetics, solar energy conversion, battery storage	44 Waterloo Rd, Room G18

Learning Outcomes

1. Distinguish the main technical features of electrical and electronic technologies used in renewable energy and storage, electrical transportation, robotics and autonomous systems
2. Identify operational characteristics of typical power converters and electrical machines for a range of industrial applications
3. Demonstrate fundamental knowledge in power computations in AC systems
4. Explain the working principles of key nonlinear devices such as transistors and power semiconductors
5. Design, simulate, and perform hardware evaluation of circuits with one or more nonlinear components

Main Focus of Part 1

Learning Outcome 4


4. Explain the working principles of key nonlinear devices such as transistors and power semiconductors

- Building on prerequisite knowledge (ELEC2070)
- Learn the properties and characteristics of non-linear devices including diodes and transistors
- Learn how these devices work at the circuit level to modify current and voltage
- Use equivalent circuit models to simplify complex linear and nonlinear circuits
- In most cases, such models can enable linearization of the circuit within the limits of interest

Learning Outcome 5

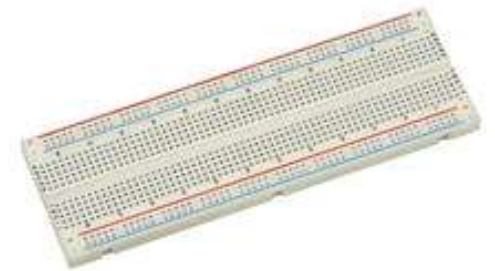5. Design, simulate, and perform hardware evaluation of circuits with one or more nonlinear components

- Throughout the unit you will use LTSpice circuit simulation tools to help build your understanding of non-linear devices and circuits
- This learning outcome will be assessed in the laboratory sessions. Lab 1 will include an introduction to circuit simulation with LTSpice
- To work through the Part 1 lab worksheets you will build and analyse physical electronic circuits
- You will learn how to rapidly prototype non-linear circuits and how to measure the response (steady state and frequency response)



Assessment

- Assessment will be split across pre-lecture mini-quizzes, laboratory sessions, online assignments, and a final exam
- Weekly schedule gives details of relevant timings and deadlines
- Further details will be available through iLearn

Assessment Type	Assessment Weightings (%)
Pre-lecture mini quizzes	10
Laboratories	25
Assignments	30
Final Exam	35

Pre-Lecture Mini Quizzes


- A short ilearn quiz will be made available in the week prior to each lecture
- Lecture slides and additional learning content for that week will also be available on iLearn
- You will use these resources to answer the mini-quiz **before** coming to the lecture (The quiz will close at the lecture start time!)
- This is to encourage active student engagement and better understanding during the lectures
- These quiz questions will be short and simple. They will total 10% of the overall assessment for the unit.

Laboratories and Workshops

Aligned with learning outcomes.

1. Laboratory sessions for simulating, constructing and measuring circuits.
2. Problem solving workshops for practicing for tests.

Start in **Week 2** (check weekly plan)

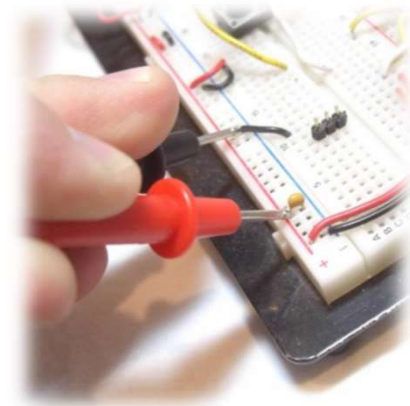

To maximize benefit,
arrive on time to
scheduled sessions
and use your time
efficiently



Revise lecture notes
and online learning
content to prepare



You can work on labs
or tutorials in your
own time, during the
timetabled session,
or both!



Upload your lab
worksheet
questions to iLearn
for grading.

Flexible Practical Learning

- Part 1 Laboratory modules are in a worksheet format
- You will be provided with portable 'lunch-box lab kits'
- You can progress through the worksheets on your own schedule, in the location of your choice
- During scheduled lab timeslots we will provide support
- It is strongly recommended that you attend these sessions
- You should at least carry out the 'pre-lab' section of the worksheet before attending scheduled lab session
- Worksheet answers will be submitted via an ilearn quiz

Deadline is 11:55pm on the day of the scheduled lab session (unless stated otherwise)



Collect kits this week! See iLearn for instructions


Assignments

-
- Assignment questions will be in the form of iLearn quizzes.
 - Questions will have randomised component values (answers will vary – Do not copy each other!)
 - Your marks and the correct answers will be posted < 2 weeks after the submission date
 - You will have at least 10 days to complete each assignment! Late submissions will only be accepted through formal special consideration requests with evidence.
 - Worked solutions will not be provided by default. If one of your answers is marked incorrect, you are encouraged to re-work the problem to try to find the error and get to the correct answer
 - The conveners and tutors are here to help if needed, we will happily work through it with you

Interactive Feedback

Poll Everywhere

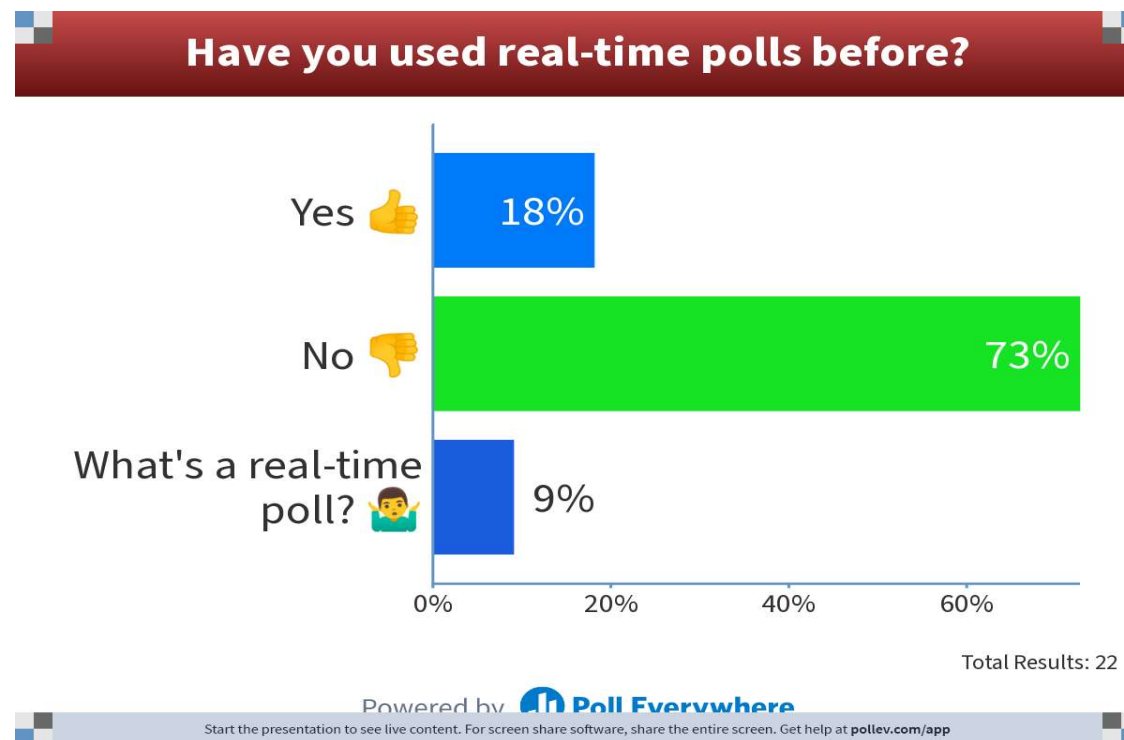- We use Poll Everywhere for real-time feedback and polling during lectures
- Use your browser in smartphone/computer or install the Poll Everywhere App



Timer Bar
(2 mins)



Go to **PollEv.com/davidpayne187** on your mobile or laptop to vote




Lecture 1


1. Unit Overview
2. **Review of fundamental concepts**
3. Nonlinearity
4. Amplifiers

Review of Fundamentals

POLARITY, RESISTANCE

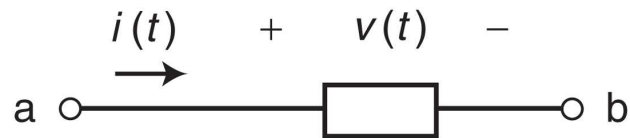

(a)

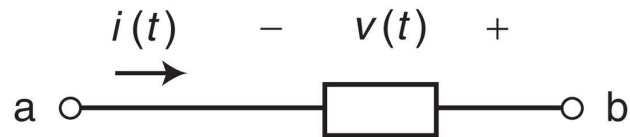

(b)

(a) **Passive:** Cannot introduce net energy into the circuit (for example a resistor).

(b) **Active:** Relies on a source of energy – can usually inject power to the circuit (for example a battery).

We are going to use resistors in their linear region


$$v = Ri$$



Mathematical model of an ideal (linear) resistor


Review of Fundamentals

IDEAL INDEPENDENT SOURCES

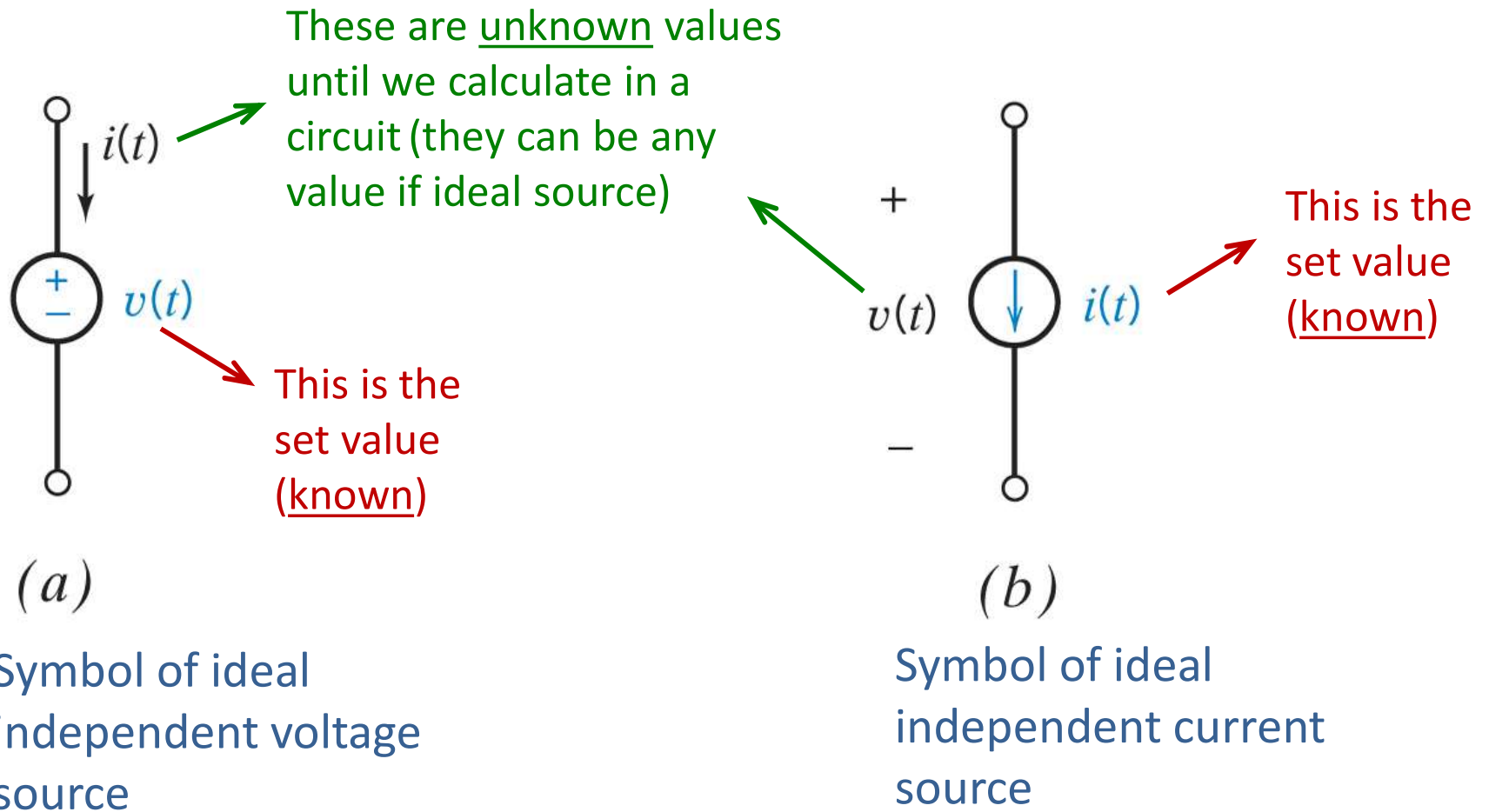


Review of Fundamentals


DEPENDENT SOURCES

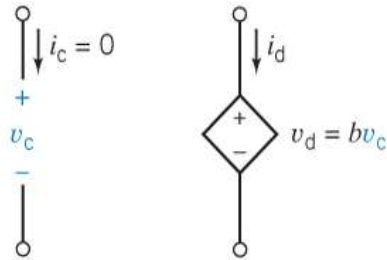


Voltage-Controlled
Voltage Source (VCVS)

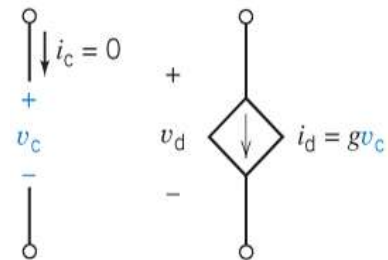

Voltage-Controlled
Current Source (VCCS)

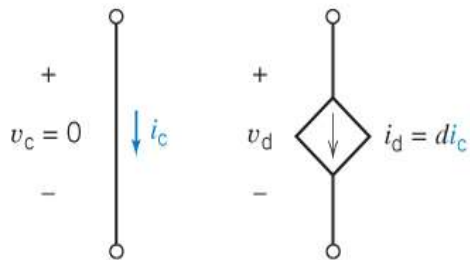

Current-Controlled
Current Source (CCCS)

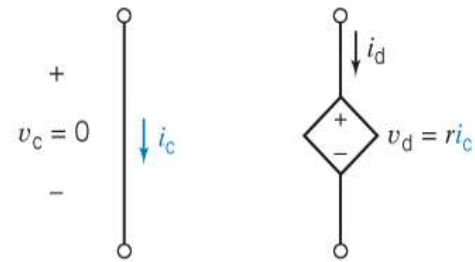


Current-Controlled
Voltage Source (CCVS)

There are no simple dependent sources in practice!
But they are useful for modelling transistors, amplifiers etc.

Review of Fundamentals

DEPENDENT SOURCE EXAMPLE

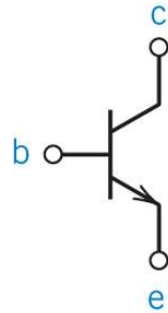
Transistor action:
Current between **c** and **e** depends on voltage between **b** and **e**




(a)

$$i_c = g_m v_{be}$$

↑
constant

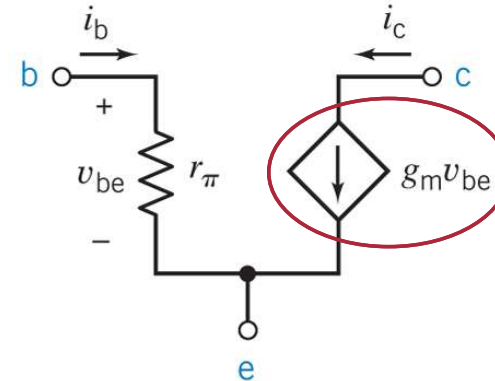


(b)

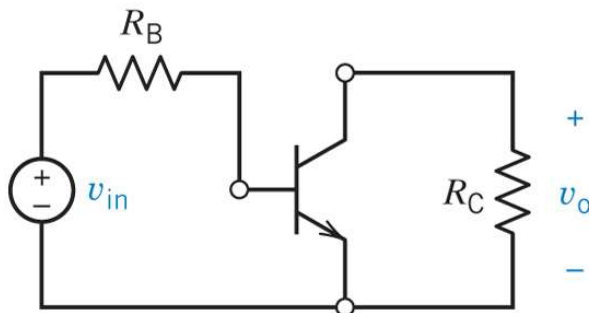

(c)

Actual circuit

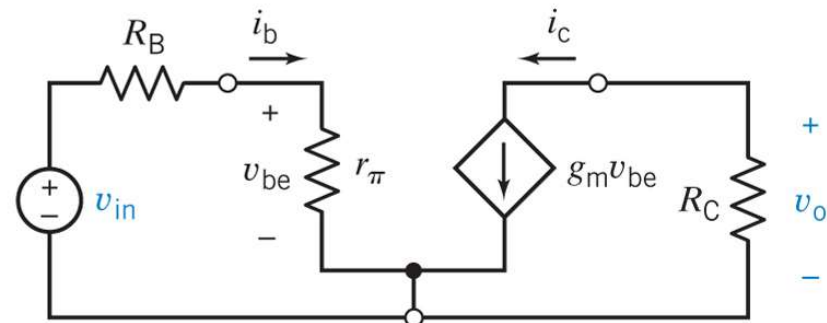

(d)


Equivalent circuit

- easier to analyze
- describes behavior of original circuit

Review of Fundamentals


KIRCHOFFS LAWS

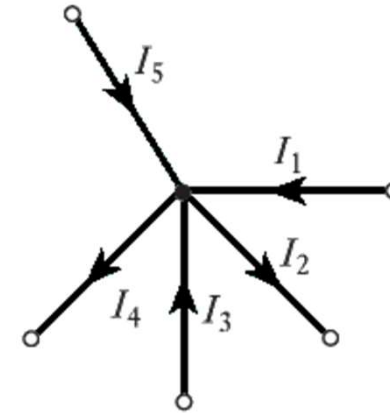The algebraic sum of all **currents entering or leaving a node** is zero at any time instant



$$I_1 - I_2 + I_3 - I_4 + I_5 = 0$$

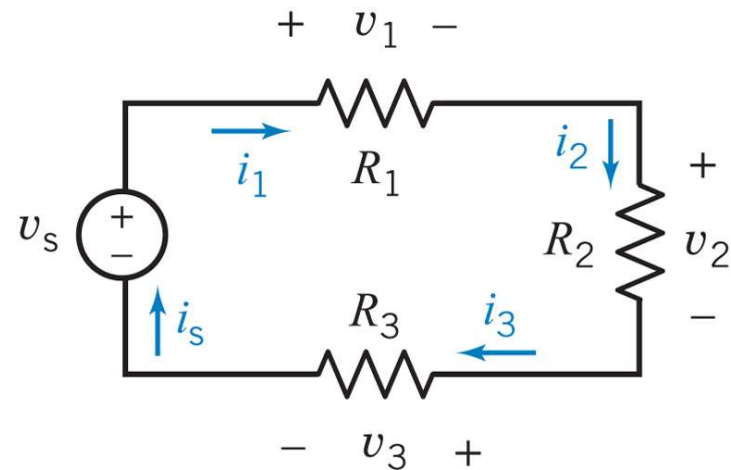
The algebraic sum of all **voltages around a loop** is zero at any time instant



$$v_1 + v_2 + v_3 - v_s = 0$$

Review of Fundamentals


NODES

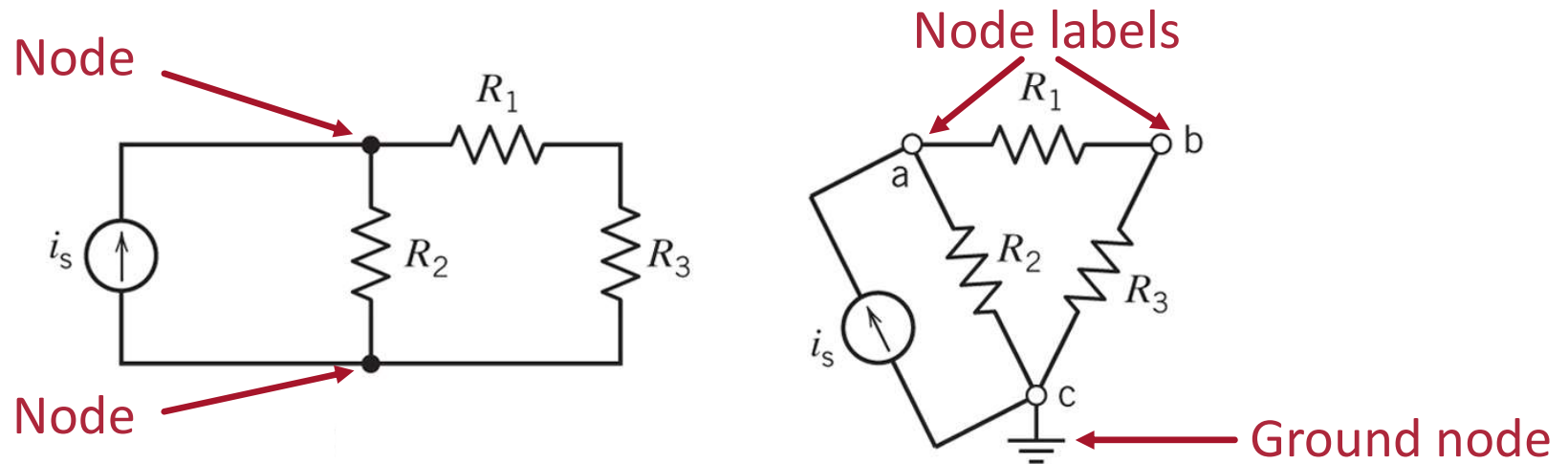

Ground node potential is zero volts.




All other nodes can be measured relative to ground.

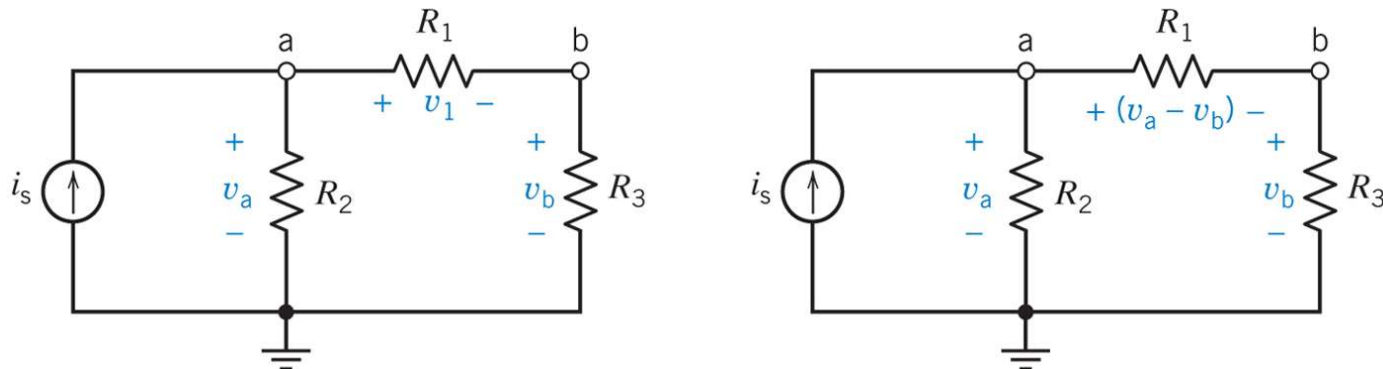Each node corresponds to a unique voltage (relative to ground).



Review of Fundamentals

NODE VOLTAGE ANALYSIS: STEP 1

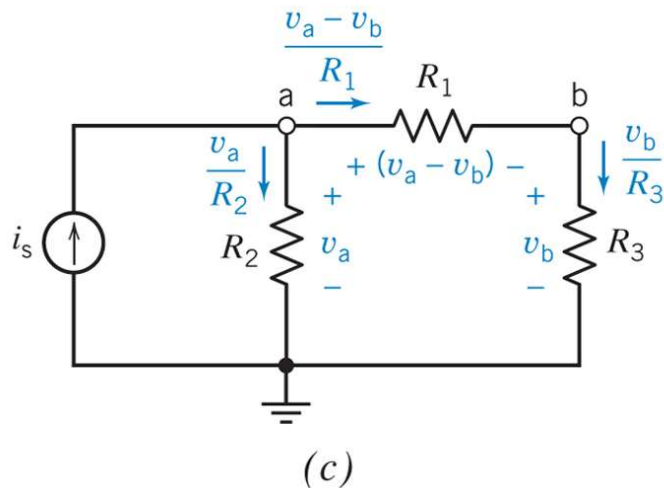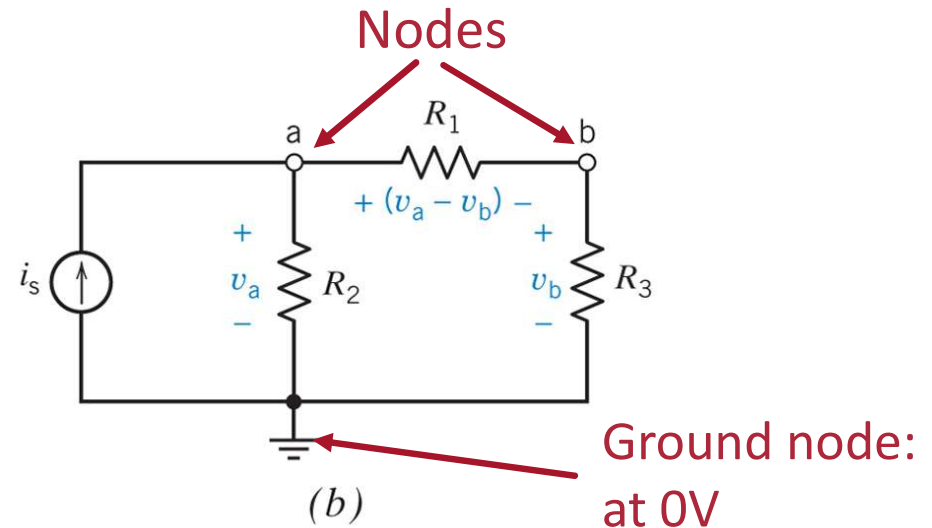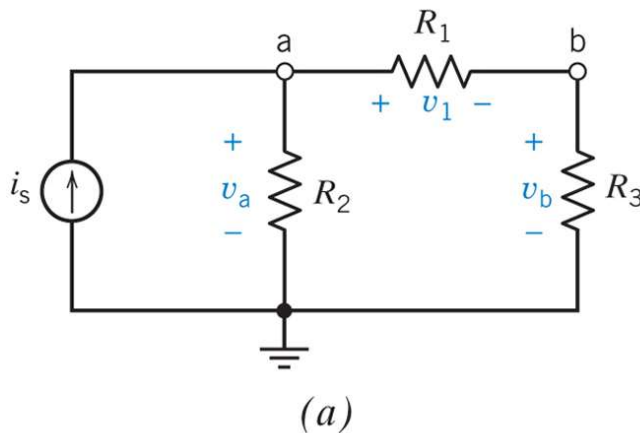

1. First, write element currents in terms of node voltages:


$$i_1 = \frac{v_a - v_b}{R_1} \quad i_2 = \frac{v_a}{R_2} \quad i_3 = \frac{v_b}{R_3}$$

Pay attention to the direction of current!

Review of Fundamentals

NODE VOLTAGE ANALYSIS: STEP 2

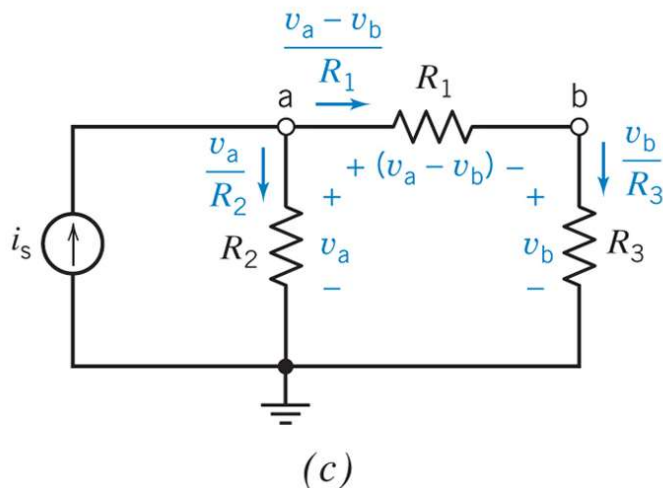2. Apply Kirchhoff's **Current** Law at each node, except for the ground node:



Node a: $i_s = i_1 + i_2$

$$i_s = \frac{v_a - v_b}{R_1} + \frac{v_a}{R_2}$$

Node b: $i_1 = i_3$


$$\frac{v_a - v_b}{R_1} = \frac{v_b}{R_3}$$

The variables i_1 and i_2 are not needed if we want to find only the node voltages. The source current i_s is normally given.

Review of Fundamentals

NODE VOLTAGE ANALYSIS: STEP 3

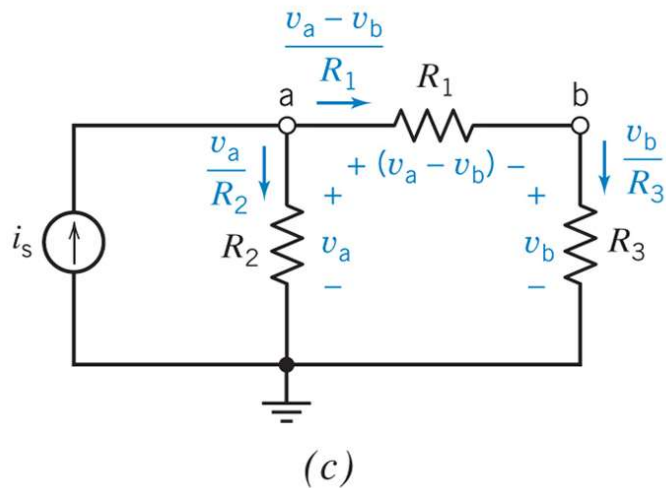3. Order the equations with respect to the unknowns (such as you would do for the matrix method) and solve them:



Node
a:

$$i_s = \frac{v_a - v_b}{R_1} + \frac{v_a}{R_2}$$

$$i_s = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) v_a - \frac{1}{R_1} v_b$$

Node
b:


$$\frac{v_a - v_b}{R_1} = \frac{v_b}{R_3}$$

$$0 = \left(\frac{1}{R_1} + \frac{1}{R_3} \right) v_b - \frac{1}{R_1} v_a$$

Review of Fundamentals

THÉVENIN'S THEOREM

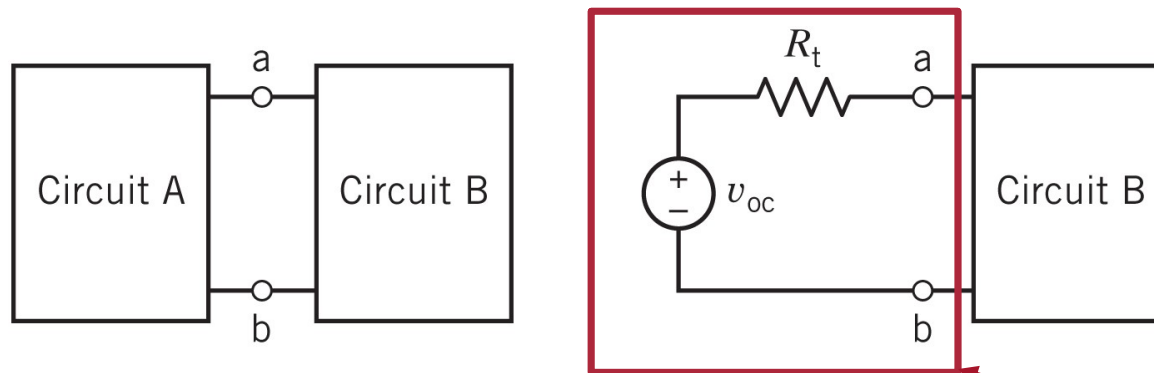“Any combination of voltage sources and resistors with two terminals can be replaced by a single voltage source and a single series resistor.”




Léon Charles Thévenin
1857 - 1926

Thévenin equivalent
circuit

Circuit A can be replaced with a
simpler Thévenin equivalent
circuit.

Review of Fundamentals

THÉVENIN'S THEOREM

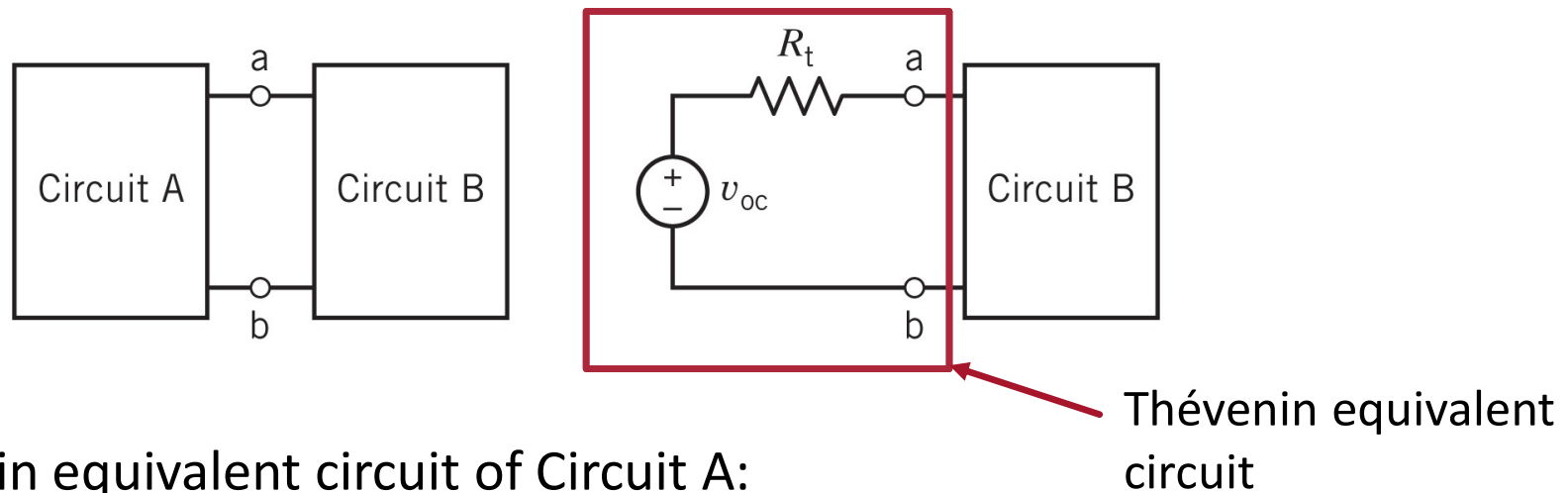

Thévenin equivalent circuit of Circuit A:

1. Calculate the **open-circuit voltage** and the **short-circuit current** of Circuit A.


2. Then calculate Thévenin resistance as:
$$R_t = \frac{v_{oc}}{i_{sc}}$$

This method works well for calculations but may not be good in practice.

For example: if you short circuit a battery, you will discharge it.

Review of Fundamentals

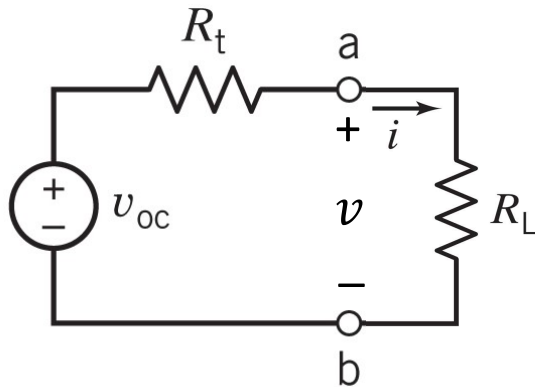
GRAPHICAL ANALYSIS TO DETERMINE THÉVENIN EQUIVALENT



From KVL we have

$$v = v_{oc} - R_t i$$

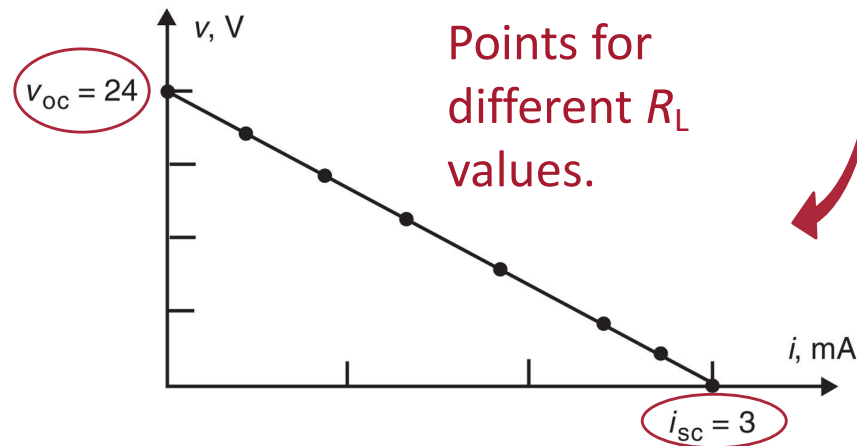Only v_{oc} and one R_L measurement is needed to make a linear graph. This is easy.



A plot of terminal voltage and currents.

Useful method for
when we are in
the lab!




Lecture 1


1. Unit Overview
2. Review of fundamental concepts
3. **Nonlinearity**
4. Amplifiers

Intro to Nonlinear Devices

DEVICES

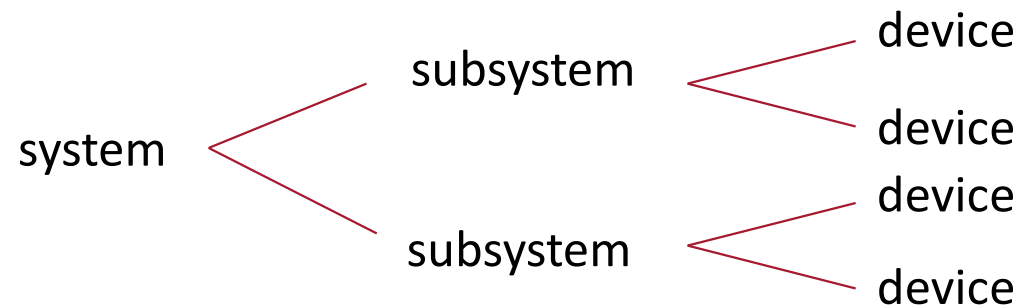


Example case:

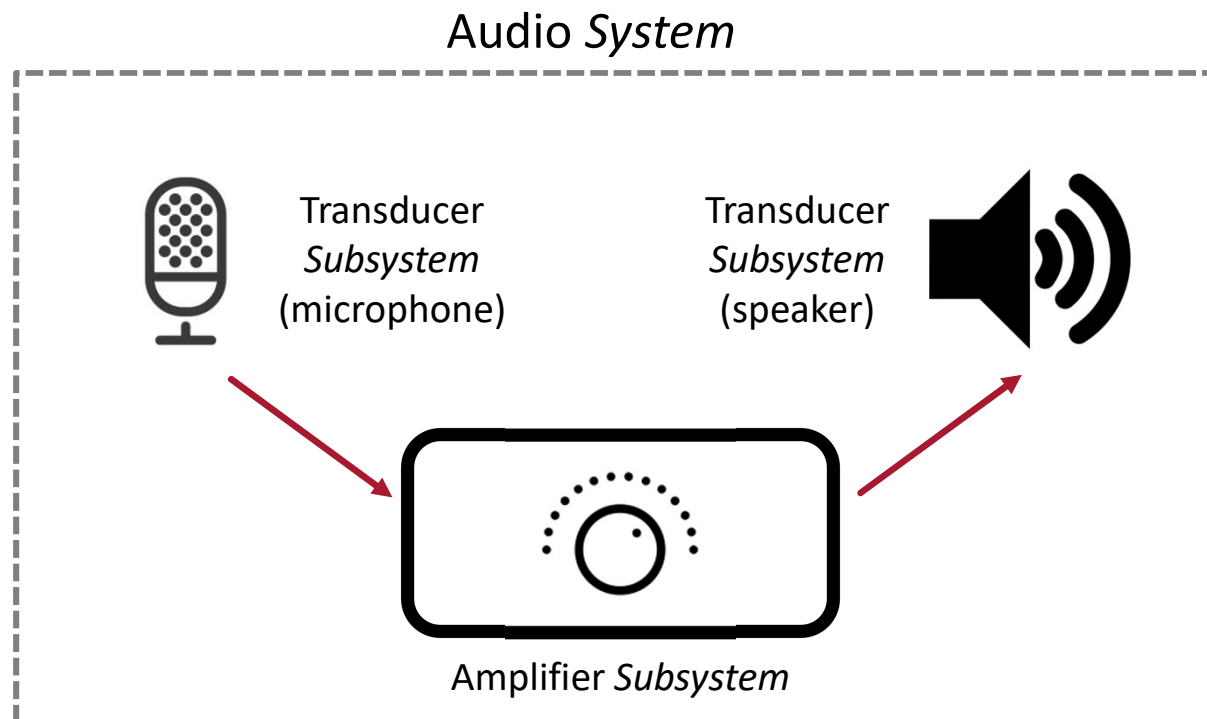

Intro to Nonlinear Devices


Devices

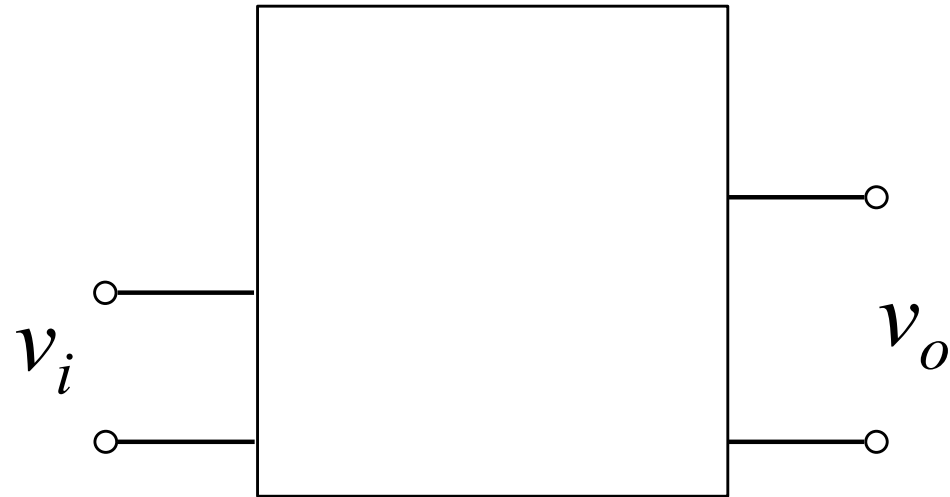

Amplifier subsystem

Intro to Nonlinear Devices


Devices

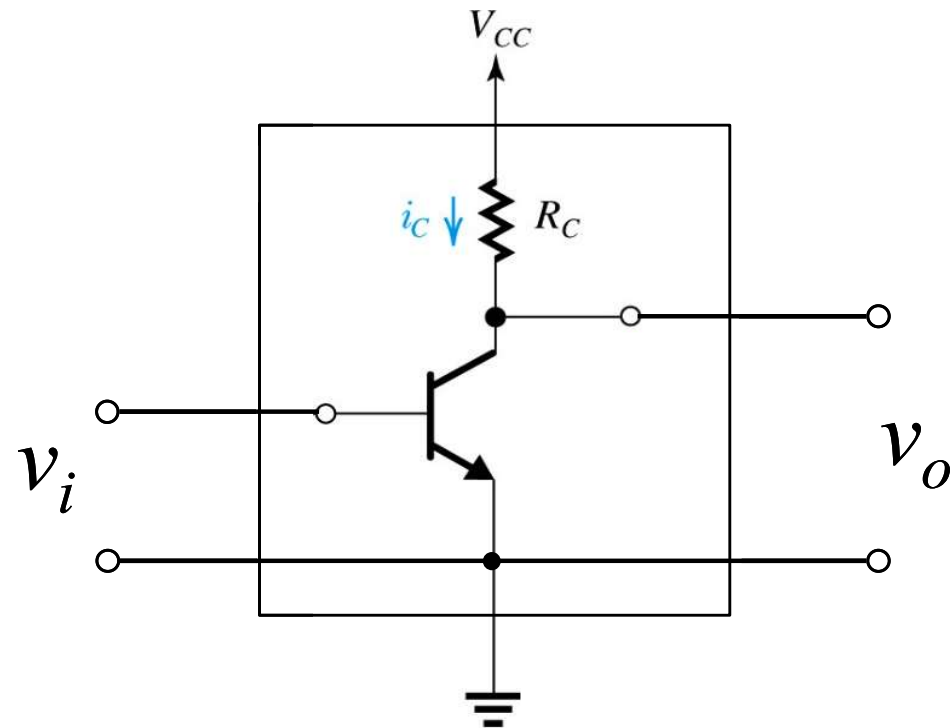

Amplifier subsystem

Intro to Nonlinear Devices

Devices

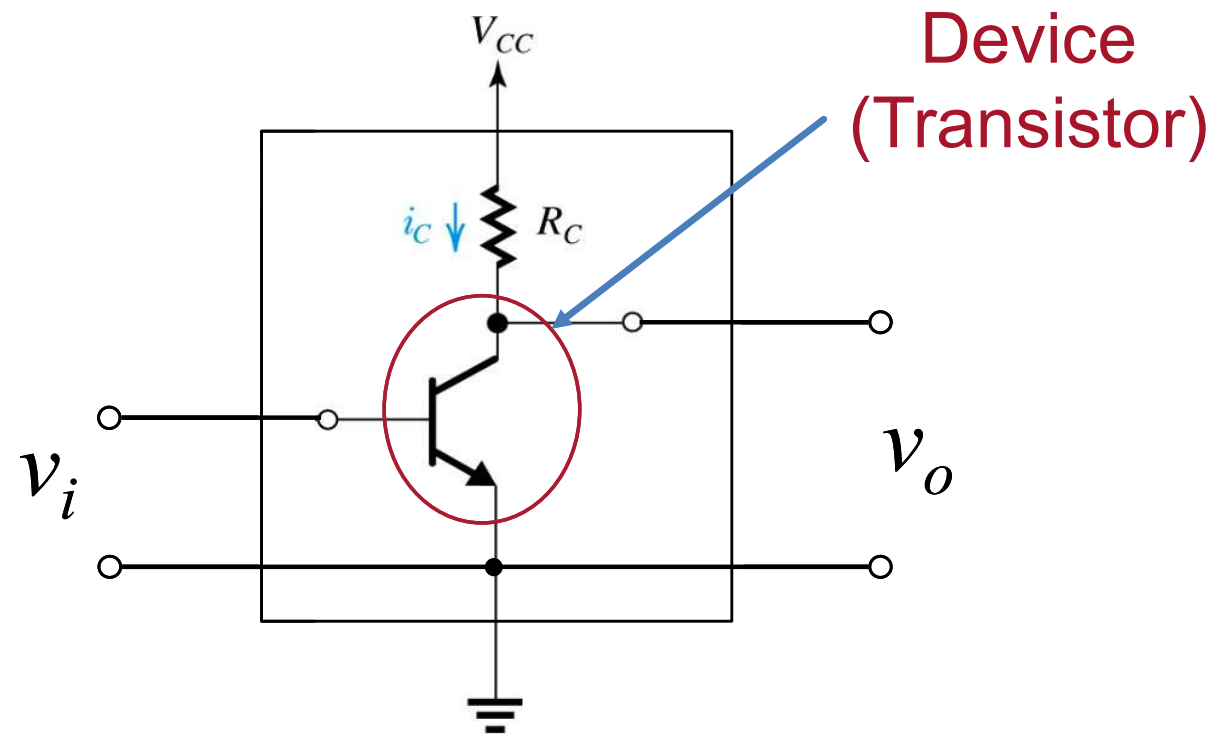


Amplifier subsystem

Intro to Nonlinear Devices

WHAT IS A NONLINEAR DEVICE/CIRCUIT?

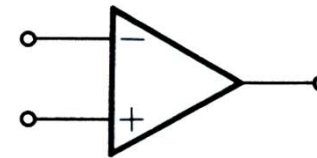
- Many systems/subsystems involve complex nonlinear circuits with multiple nonlinear devices
- Four of the most common nonlinear devices are shown here, diodes and transistors and the circuits constructed with them are the focus of part 1 of this unit
- For each of these, the relationship between their output and input characteristics is not linear




Opamp



Diode

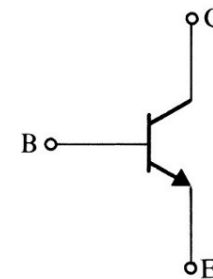

Bipolar Junction
Transistor


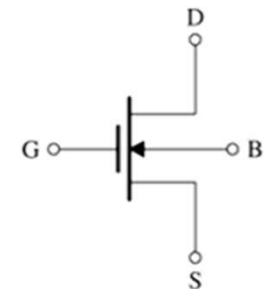


Field Effect
Transistor

Intro to Nonlinear Devices

WHAT IS A NONLINEAR DEVICE/CIRCUIT?

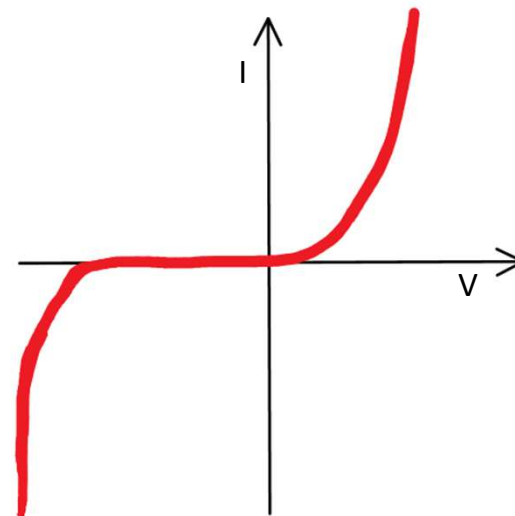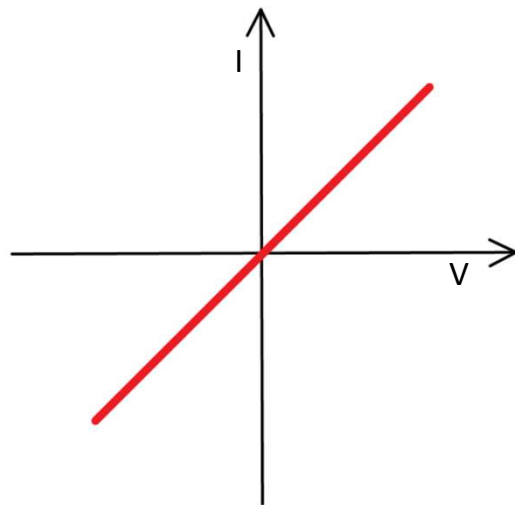
- Devices such as *ideal* resistors, capacitors and inductors have a output characteristics that are a linear function of input.
- Diodes and transistors have a more complex relationship between input and output
 - Though they have regions of linearity



Intro to Nonlinear Devices

WHY ARE NONLINEAR DEVICES IMPORTANT?

- Much of modern electronics now involves digital signal processing and logic circuits
- However, digital electronics need to interface with the real world
- Nonlinear devices and circuits are required for this, particularly for signal amplification and initial filtering

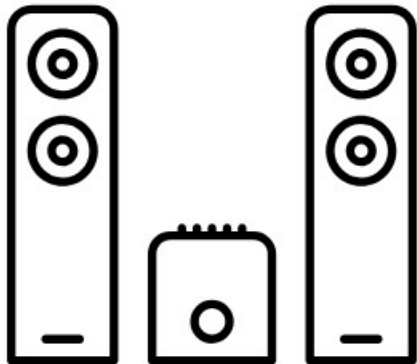



Lecture 1


1. Unit Overview
2. Review of fundamental concepts
3. Nonlinearity
4. **Amplifiers**

Amplifiers

WHY DO WE NEED THEM AND WHAT DO THEY DO?

- Most transducers produce very weak signals (uV – mV range).
- We need to strengthen these signals whilst maintaining the information
 - Need linear gain, though non linearity here can also be useful

Audio System

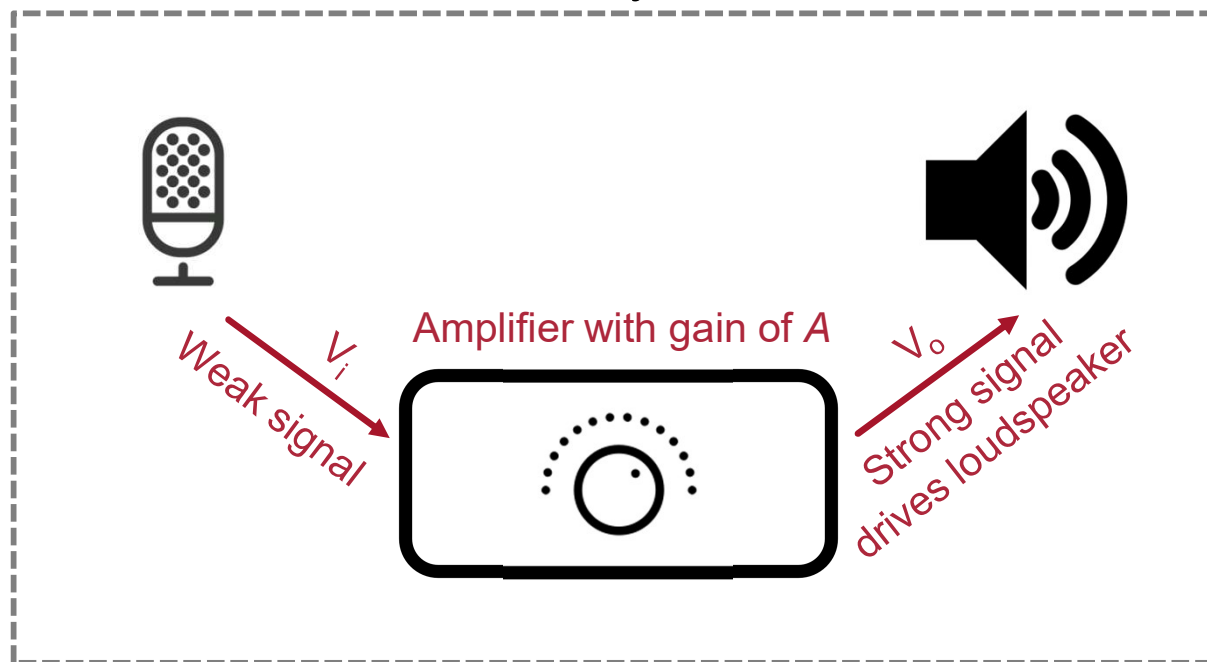


The output is the input, scaled by A (the *gain*)



$$V_o(t) = AV_i(t)$$

Amplifiers

CIRCUIT SYMBOL

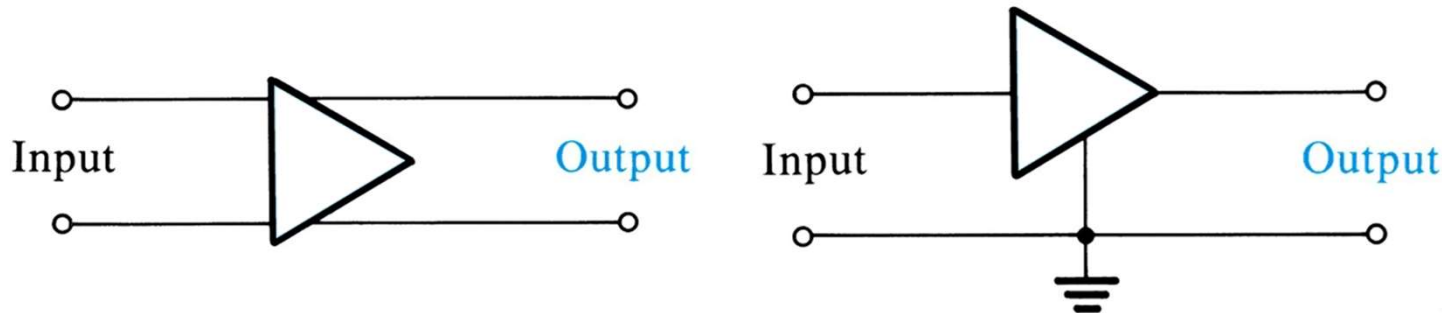

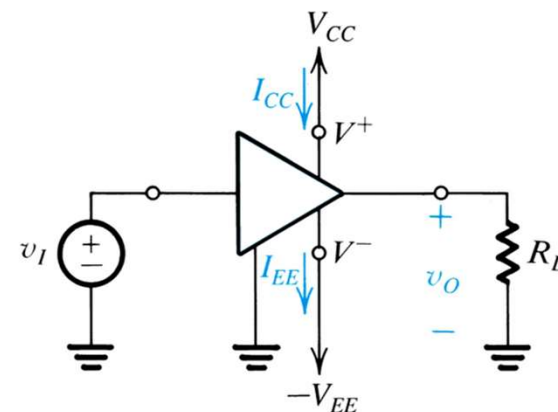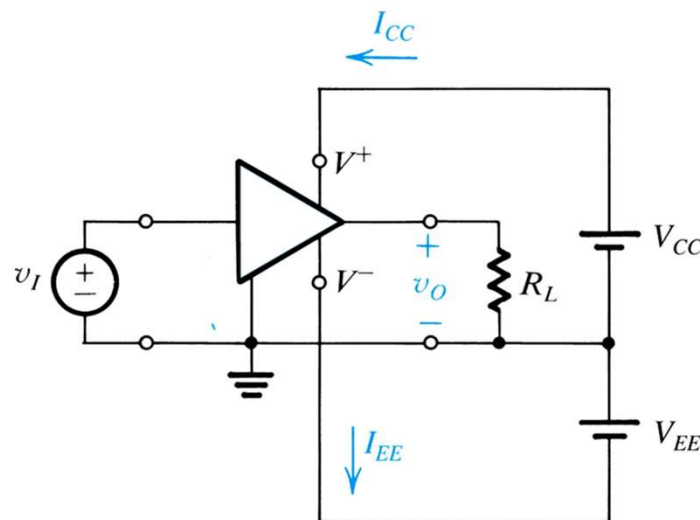
- A two port circuit, shown as a triangle indicating the direction of signal flow
- Typically there is a common terminal – a reference point (*ground*)
- In reality, the amp also has a power supply (often not explicitly shown)



Amplifiers

GAIN AND TRANSFER CHARACTERISTIC

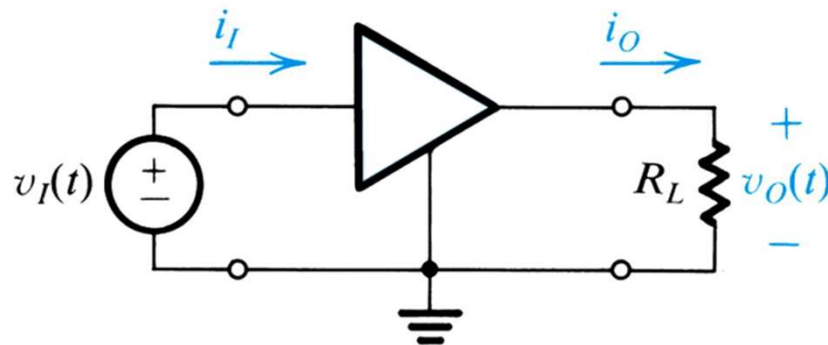- Signal gain can be achieved and expressed through voltage, current or power



Voltage gain:

$$A_v \equiv \frac{v_o}{v_I}$$

Current gain:

$$A_i \equiv \frac{i_o}{i_I}$$

Power gain:

$$A_p \equiv \frac{v_o i_o}{v_I i_I} = A_v A_i$$

Gain is a ratio, expressed as dimensionless, or V/V, A/A etc.


Engineers often express gain logarithmically

$$20 \log |A_v| \quad \text{dB}$$

$$20 \log |A_i| \quad \text{dB}$$

$$10 \log A_p \quad \text{dB}$$

Example transfer characteristic:

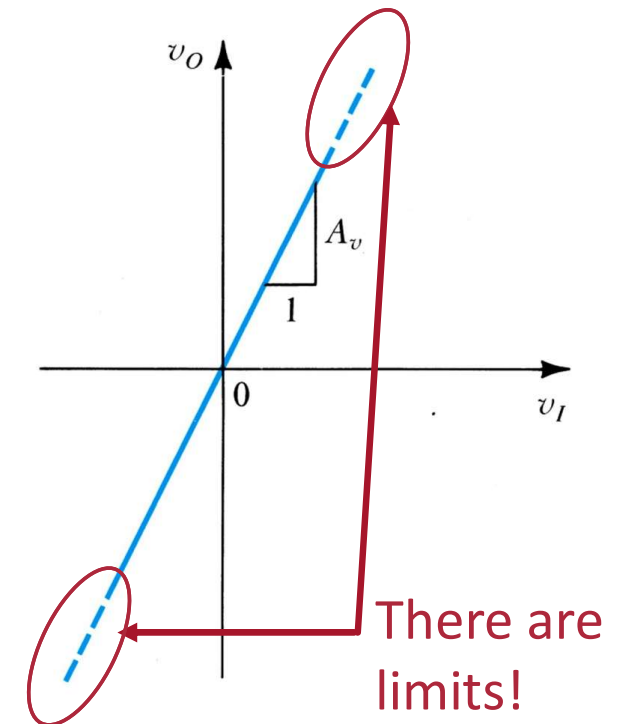


Amplifiers

SATURATION

- In reality, gain is limited
- Saturation, or clipping, will occur when the output voltage approaches that of the power supplies
- Output signal becomes distorted

We must design amplifiers to avoid this! Knowledge of the input range is needed.



More realistic transfer characteristic

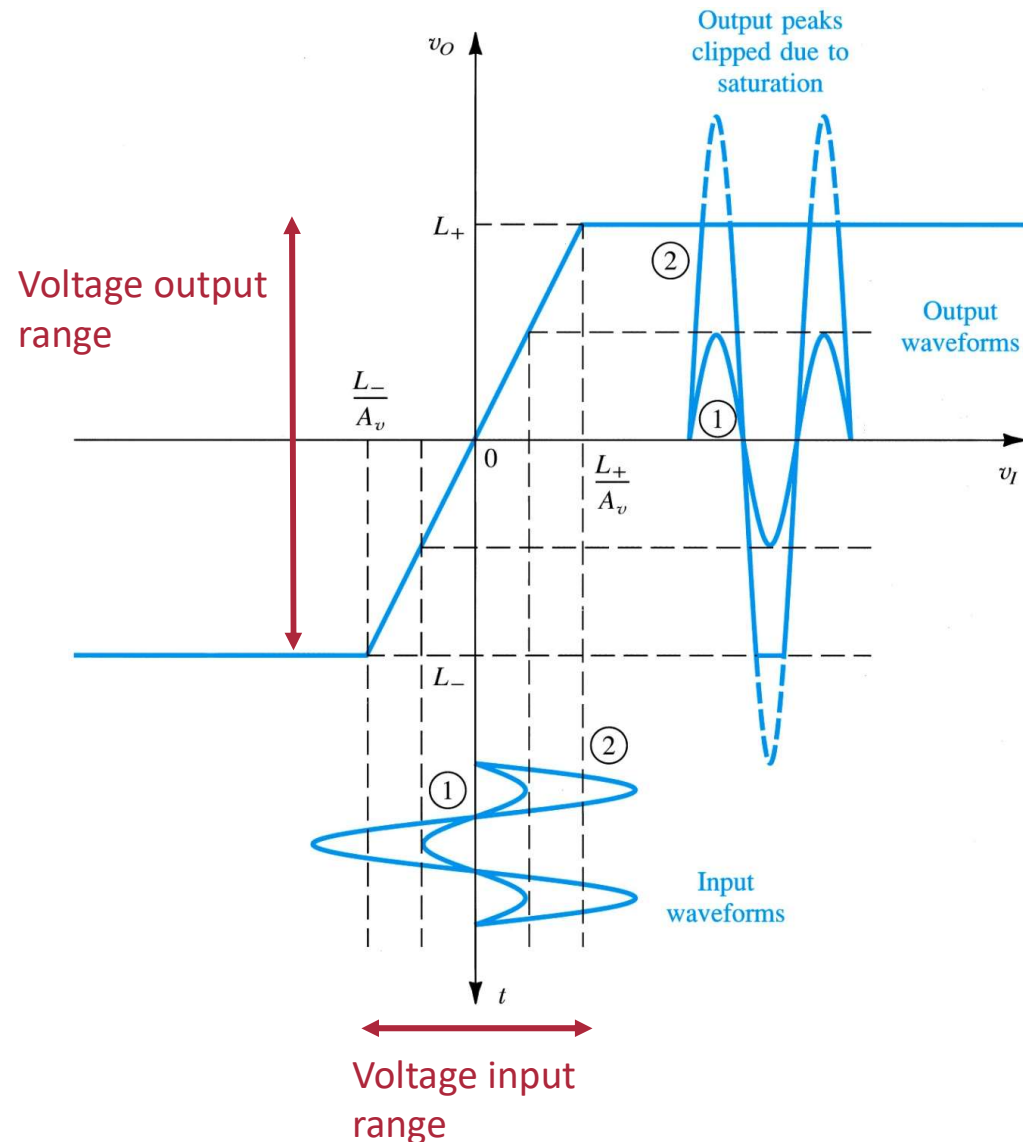

Amplifiers

FREQUENCY RESPONSE AND BANDWIDTH

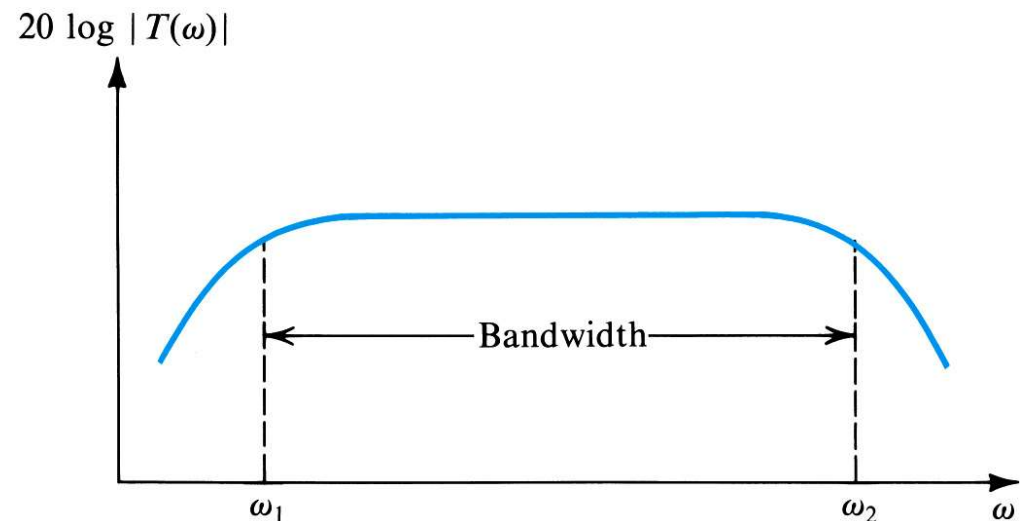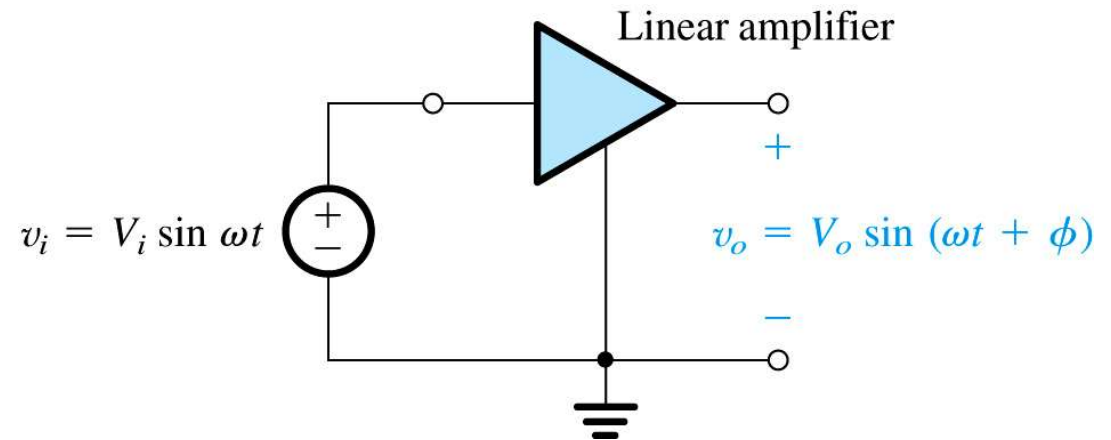- Amplifying a sine wave signal can change its amplitude and phase, but not its frequency
- Amplifiers typically only have a flat gain response over a specific frequency range, the *bandwidth*





We must design amplifiers to operate correctly over the correct frequency range for our application!

Amplifiers

CIRCUIT MODELS

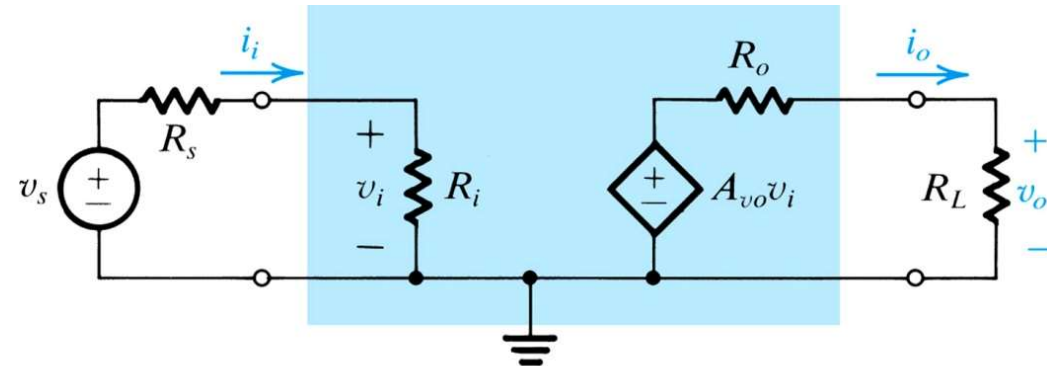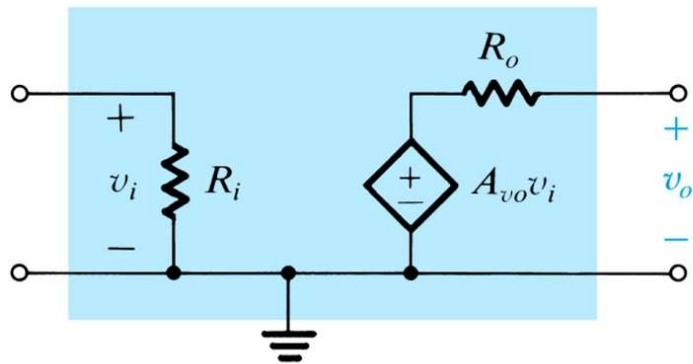- Used to model terminal behaviour of amp (simplified to a building block)
- Example for a voltage amplifier



Open circuit voltage
gain:

$$A_{vo} = \frac{v_o}{v_i}$$

$$v_o = i_o R_L = A_{vo} v_i R_L / (R_o + R_L) = A_{vo} v_i \frac{R_L}{R_L + R_o}$$

$$v_i = v_s \frac{R_i}{R_i + R_s}$$

Overall voltage gain:

$$\frac{v_o}{v_s} = A_{vo} \frac{R_i}{R_i + R_s} \frac{R_L}{R_L + R_o}$$


Amplifiers

THE FOUR TYPES OF AMPLIFIER

- Signal of interest (at input or output) may be current or voltage
- Voltage amplifier is most popular but other models can be used


Voltage Amp

$$A_{vo} \equiv \left. \frac{v_o}{v_i} \right|_{i_o=0} \quad (\text{V/V})$$

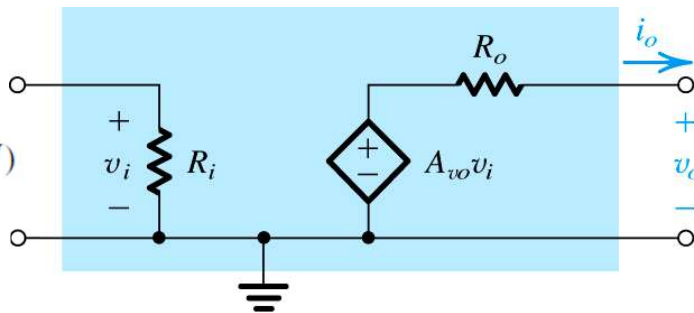


Current Amp

$$A_{is} \equiv \left. \frac{i_o}{i_i} \right|_{v_o=0} \quad (\text{A/A})$$

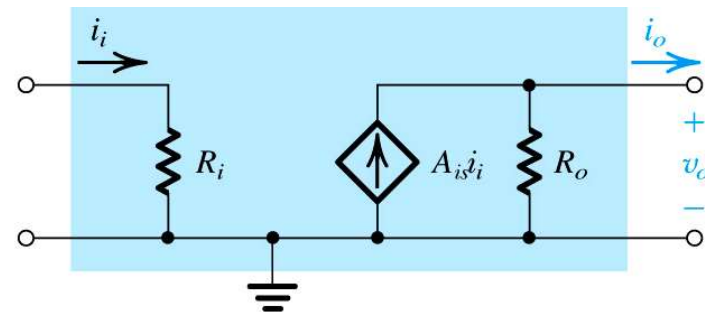


Transconductance Amp

$$G_m \equiv \left. \frac{i_o}{v_i} \right|_{v_o=0} \quad (\text{A/V})$$

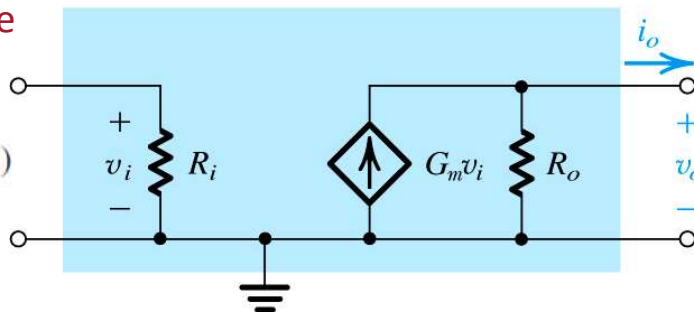


Transresistance Amp

$$R_m \equiv \left. \frac{v_o}{i_i} \right|_{i_o=0} \quad (\text{V/A})$$

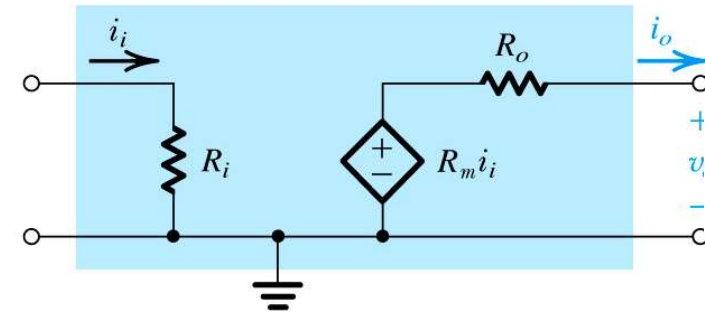

Class Example

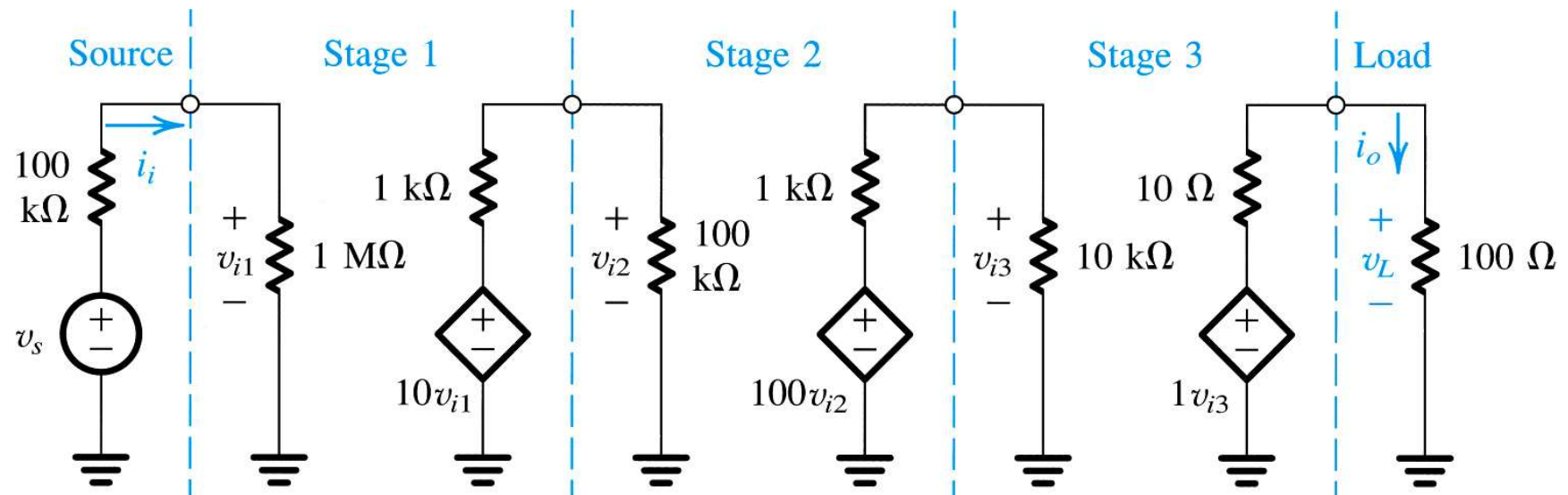CALCULATE THE GAIN OF A 3 STAGE AMPLIFIER



Class Example

CALCULATE THE GAIN OF A 3 STAGE AMPLIFIER

- just several potential dividers!
- solve one at a time
- we want the gain $\frac{V_L}{V_S}$ so need to calculate V_L in terms of V_S .

Start with v_{i1}

$$v_{i1} = v_s \times \frac{1M}{1M + 100k} = v_s \times \frac{1M}{1.1M} = 0.9090 v_s$$

next we find v_{i2}


$$v_{i2} = 10 v_{i1} \frac{100k}{101k} = 9.9 v_{i1} = 9 v_s$$

because \rightarrow
gain is 10 for this stage

now for v_{i3}

$$v_{i3} = 100 v_{i2} \frac{10k}{11k} = 90.9 v_{i2} = 818 v_s$$

gain for stage 2 is 100

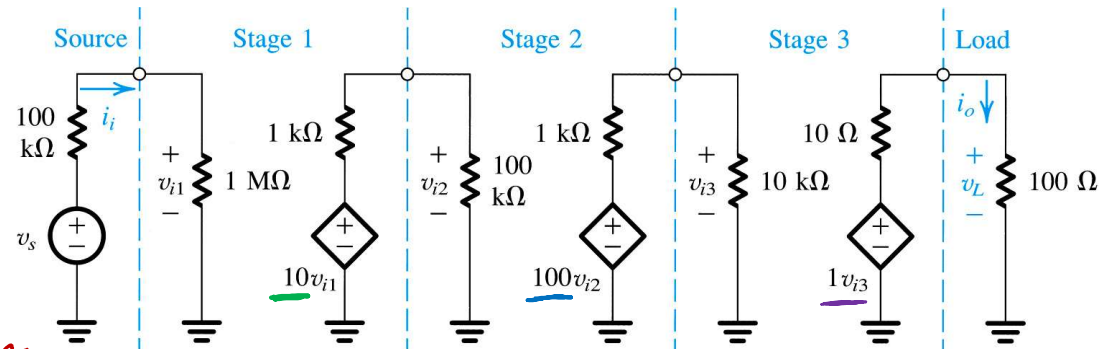

finally v_L

$$v_L = i v_{i3} \frac{100}{110} = 0.909 v_{i3} = 744 v_s$$

$$\text{So } V_L = 744 v_s$$

$$\therefore \frac{V_L}{V_S} = 744 \quad \leftarrow \text{the overall gain!}$$

What is this in dB?

$$20 \log |744| = \underline{\underline{57.4 \text{ dB}}}$$



Lecture 1

1. Unit Overview
2. Review of fundamental concepts
3. Amplifiers
4. **Prep for Lab 1**

Preparation for Lab 1

INTRODUCTION TO LTSPICE SIMULATION AND THE AD2

- You will be using LTspice to model some simple circuits
- You will build and measure these circuits on your breadboard using the Analog Discover 2 (AD2).

Preparation before the timetables lab session:

- Collect lunch-box lab kits
- Read lab module-1 worksheet (available on iLearn)
- Carry out the pre-lab tasks
- Install 'Ltspice' and 'Waveforms' on your personal computer